



K24P 3919

Reg. No. :

Name :

I Semester M.Sc. Degree (C.B.C.S.S. – OBE – Reg./Supple./Imp.)

Examination, October 2024

(2023 Admission Onwards)

PHYSICS/PHYSICS WITH COMPUTATIONAL AND NANO SCIENCE

SPECIALIZATION

MSPHN01C04/MSPHY01C04 : Electronics

Time : 3 Hours

Max. Marks : 60

SECTION – A

Answer **any 5**, **each** one carries **3** marks.

1. Outline block diagram representation of a typical OPAMP.
2. What are the differences between synchronous and asynchronous counters ?
3. What is the potential timing problem in flip-flop circuits ?
4. What are the different classifications of microprocessors ?
5. Explain the oscillator principles.
6. Summarize the different comparator characteristics. **(5×3=15)**


P.T.O.



SECTION – B

Answer **any 3**, **each** one carries **6** marks.

7.

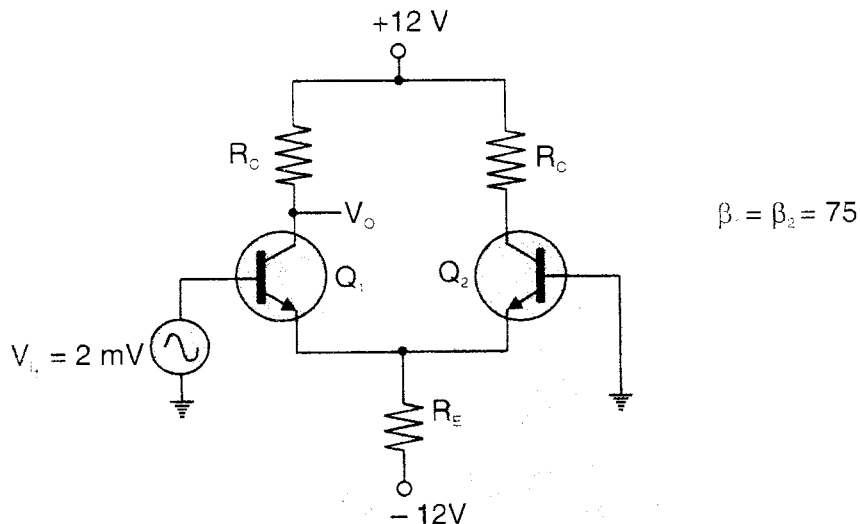

In the circuit shown, if $r_i = 20 \text{ k}\Omega$, $R_C = 72 \text{ k}\Omega$ and $R_E = 48 \text{ k}\Omega$, calculate

- Single-ended output voltage
 - Common mode gain.
- Build a J-K flipflop by using an S-R flipflop.
 - Categorize different flag registers.
 - Design a synchronous 3-bit Up-down counter using J-K FFs.
 - Make use of op-amp 1458/353 to design a triangular wave generator. **(3×6=18)**

SECTION – C

Answer **any 3**, **each** one carries **9** marks.

- Organize and explain the different functional units of the 8085 microprocessor.
- Compare and contrast R-2R ladder type DAC and weighted resistor type DAC.
- List and appraise different types of shift registers.
- Justify how the inverting, noninverting and differential configurations of OPAMP are useful in applications like summing, scaling and averaging amplifiers.
- Distinguish and explain first-order low-pass and high-pass Butterworth filters. **(3×9=27)**