

**Fourth Semester FYUGP Degree (Reg) Examination April
2026**

KU4DSCPHY204 - ELECTRONICS I

2024 Admission onwards

Time : 1.5 hours

Maximum Marks : 50

Section A

Answer any 6 questions. Each carry 2 marks.

1. What is a hole in a semiconductor?
2. What is meant by an n-type semiconductor?
3. Covert 0.347 to binary using repeated multiplication by 2.
4. Convert 0.0981 to binary using sum of weights method.
5. What is the β_{DC} of a transistor if $I_C = 20.3\text{mA}$ and $I_E = 20.5\text{mA}$?
6. Differentiate between E-MOSFET and D-MOSFET.
7. Write the truth table and Boolean expression for a 2-input NAND gate.
8. Simplify $Y = ABC + AB\bar{C} + A\bar{B}C$

Section B

Answer any 4 questions. Each carry 6 marks.

9. Draw a voltage divider circuit. Explain the loading effects in voltage-divider bias
10. A fixed bias transistor has $V_{CC} = 10\text{V}$ and $R_C = 1\text{k}\Omega$. If $V_{CE} = 4\text{V}$, find the I_C .
11. Discuss breakdown in a JFET.
12. Apply De Morgan's theorem to the expression and simplify

(a) $\overline{AB\bar{B}(C + \bar{D})}$

(b) $\overline{AB(CD + EF)}$

13. Implement the Boolean function $Y = \bar{A} + B$ using only NAND gates
14. Design a circuit to implement the Boolean expression $Y = \overline{AB + CD}$ using only NAND gates

Section C

1

Answer any 1 questions. Each carry 14 marks.

15. Explain with neat diagram the V-I characteristics of forward and reverse characteristics of a pn junction diode. Also explain the non linear property of the diode.
16. What is Binary Coded Decimal? Explain with suitable example the steps involved in adding two BCD numbers.